



ELECTRICAL TECHNOLOGY: ELECTRONICS

EXAMINATION NUMBER


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET

Attach this Answer Sheet as the last page to your Answer Book.


Complete your sketches in pen.

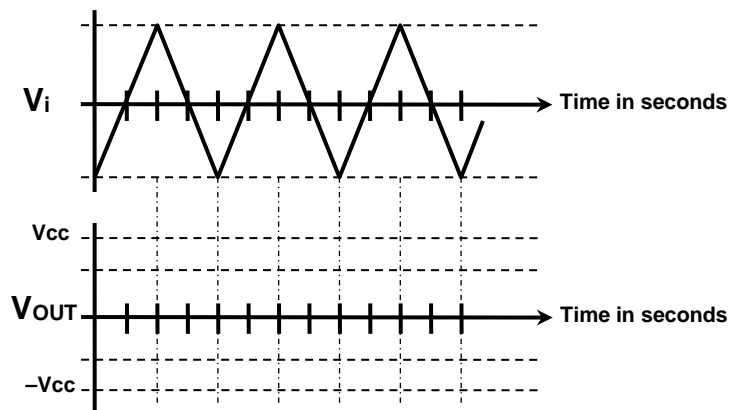QUESTION 5.5.2 SWITCHING AND CONTROL CIRCUITS




(2)

QUESTION 5.7.2

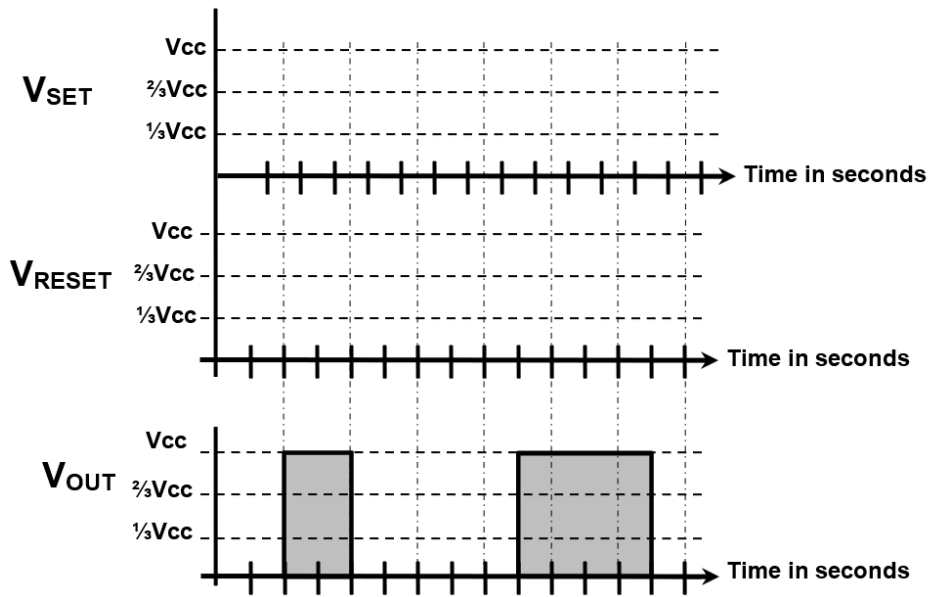

(5)

QUESTION 6.1.4 AMPLIFIERS

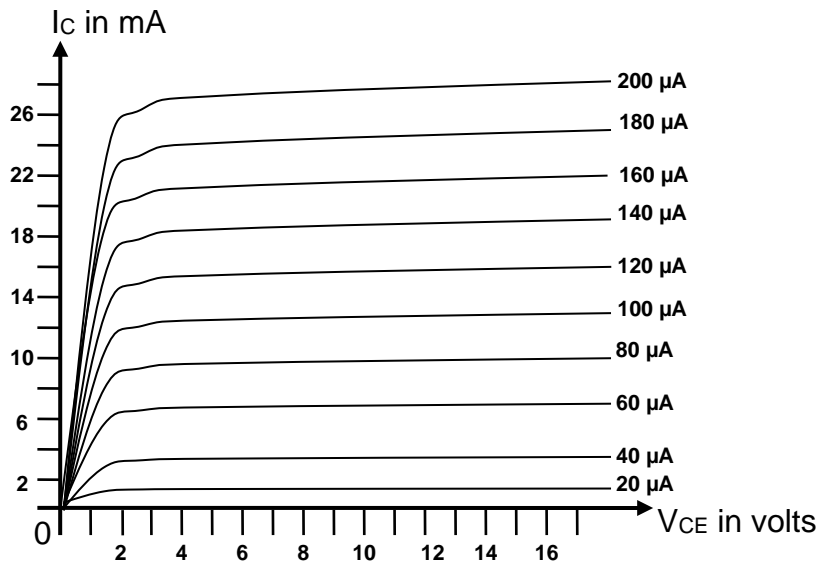

(3)