



# higher education & training

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

## **MARKING GUIDELINE**

**NATIONAL CERTIFICATE**

**DIGITAL ELECTRONICS N5**

**15 April 2021**

**This marking guideline consists of 9 pages.**



1.3

$$121,3_{16} = 001\ 010\ 001,011_2$$

$$= 1010001,011_2 \quad \checkmark$$

$$24,3_{16} = 0010\ 0100,0011_2$$

$$= 100100,0011_2$$

$$= 100100,001_2 \quad \checkmark$$


$$\begin{array}{r} \dots\dots\dots 1\ 0\ 0\ 0\ 1\ \checkmark \\ 100100001 \sqrt{1\ 0\ 1\ 0\ 0\ 0\ 1\ 0\ 1\ 1,0\ 0\ 0} \\ \dots\dots\dots \underline{1\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 1} \\ \dots\dots\dots 1\ 0\ 0\ 1\ 0\ 0\ 1\ 0\ 0\ 0 \quad \dots\dots \checkmark \\ \dots\dots\dots \underline{1\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 1} \\ \dots\dots\dots 1\ 0\ 0\ 1\ 0\ 0\ 1\ 1\ 1\ \dots\dots \\ \therefore 1010001,011_2 \div 100100,001_2 = 10,001_2 \checkmark \text{ rem } \frac{100100111}{100100001} \\ \dots\dots\dots = 2,1_8 \checkmark \dots \end{array}$$

(Final answer: 1 × 1 for correct answer and 1 × 1 for correct radix. BOTH MUST BE THERE, i.e. TWO marks or nothing.

(6)  
[18]

**QUESTION 2**

A	B	C	D	E	F	G	H
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

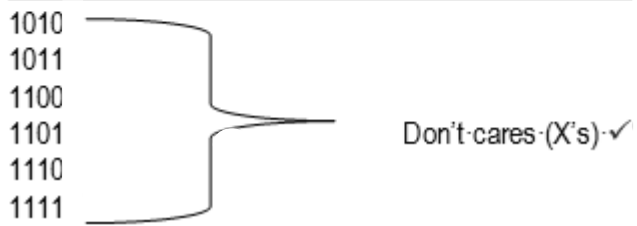

(3)

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}\bar{D}$	0	0	X	1
$\bar{C}D$	0	1	X	1
$CD$	0	1	X	X
$C\bar{D}$	0	1	X	X

$E = \bar{A} + BD + BC + \bar{B}C$  ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}\bar{D}$	0	1	X	0
$\bar{C}D$	1	0	X	1
$CD$	1	0	X	X
$C\bar{D}$	1	0	X	X

$F = \bar{B}D + \bar{B}C + B\bar{C}\bar{D}$  ✓


	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}\bar{D}$	1	1	X	1
$\bar{C}D$	0	0	X	0
$CD$	1	1	X	X
$C\bar{D}$	0	0	X	X

$G = \bar{C}\bar{D} + CD$  ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}\bar{D}$	1	1	X	1
$\bar{C}D$	0	0	X	0
$CD$	0	0	X	X
$C\bar{D}$	1	1	X	X


$H = D$  ✓

(8)

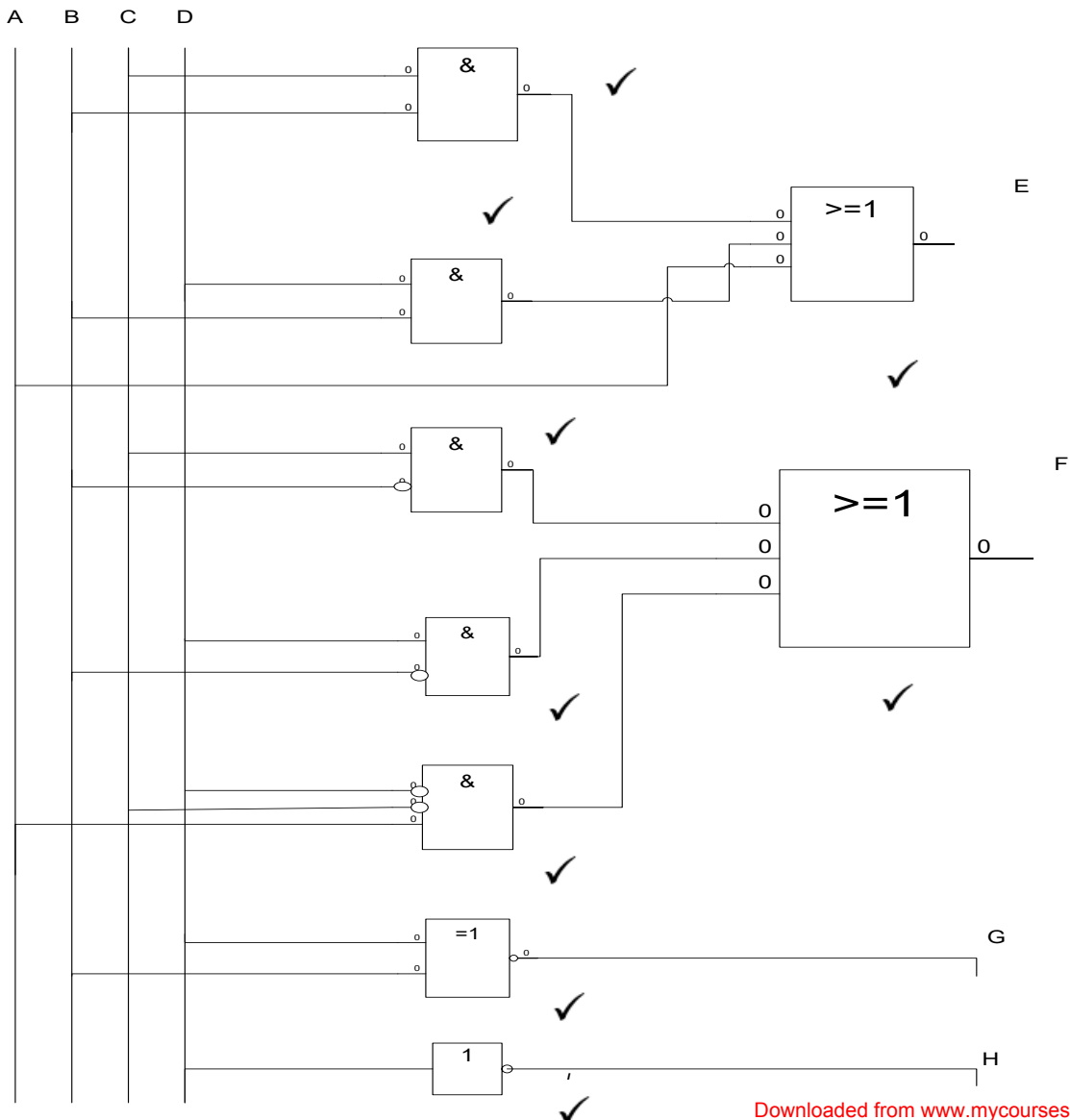


**QUESTION 3**

3.1

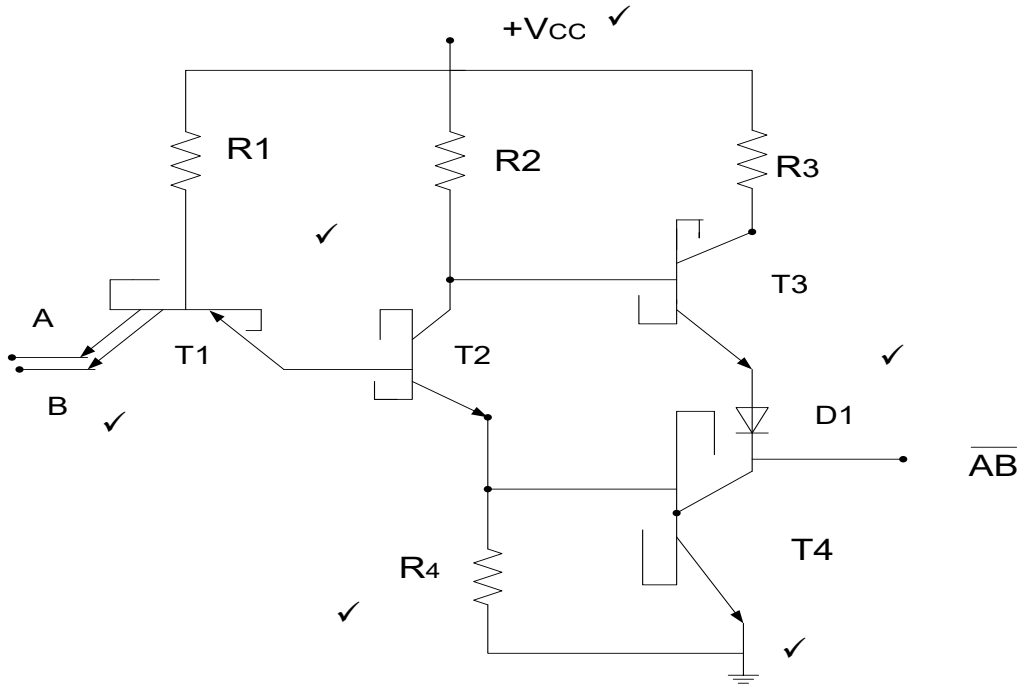

(6)

3.2

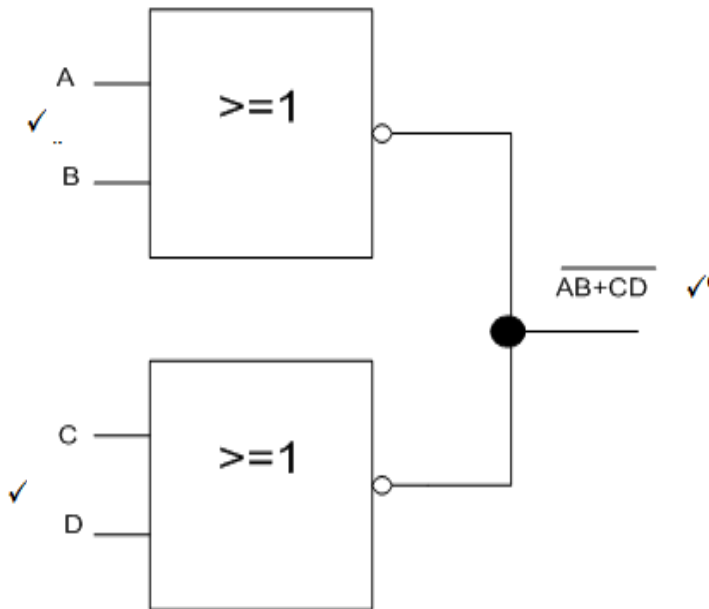

(3)


3.3 3.3.1 It is the maximum induced voltage a device can withstand without a false change in output.

3.3.2 It is the time difference between when an input is applied to a gate and when it appears at the output of the gates.

(2 × 2) (4)  
**[13]**

**QUESTION 4**

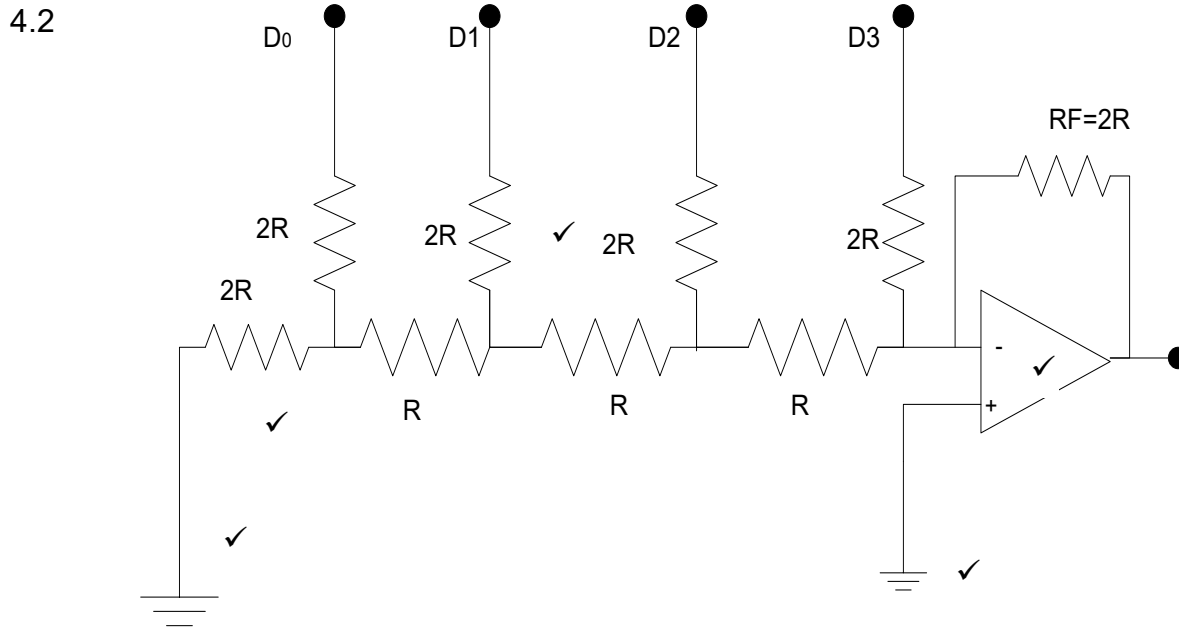4.1 
$$V_0 = \frac{A \times t \times V_{in}}{RC} = \frac{1 \times 10^{-3} \times 1 \times 3\,672}{100 \times 10^3 \times 100 \times 10^{-6}} = 0,3672 \text{ V}$$
 (3)



(NOTE: 2 × 1 marks for the correct circuit)  
 (2 × 1 marks for any correct labelled resistors)  
 (1 × 1 mark for correct op-amp) (5)

4.3 The R/2R ladder digital-to-analogue converter requires only two resistor values. (1)

4.4 
$$V_0 = \frac{V_1 + 2V_2 + 4V_4 \dots}{2^n - 1}$$
 (1)  
**[10]**

**QUESTION 5**

- 5.1      5.1.1      E  
           5.1.2      F  
           5.1.3      H  
           5.1.4      B  
           5.1.5      A  
           5.1.6      D  
           5.1.7      I  
           5.1.8      C

(8 × 1)      (8)

5.2       $\log_{m_{10}} = \log_{10} 2^n$  ✓

$\therefore \log m = n \log 2$


$\therefore n = \frac{\log m}{\log 2}$  ✓

$\therefore n = \frac{\log 16384}{\log 2}$  ✓

$\therefore n = 14$  ✓

(4)

5.3

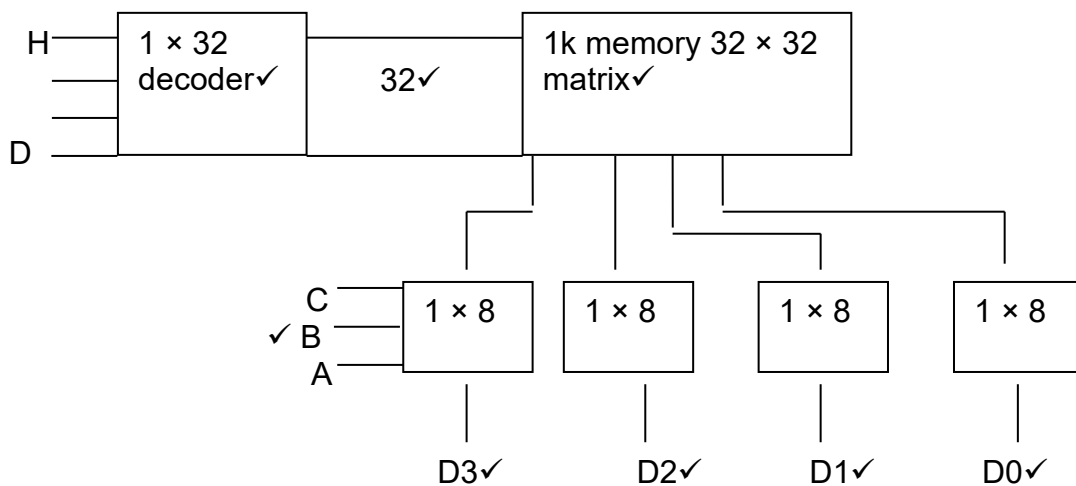

(8)  
 [20]


**QUESTION 6**

- 6.1
- Computer display
  - Printers
  - Projectors
  - Speakers
  - Game controllers
- (Any 2 × 1) (2)

- 6.2
- Keyboard
  - Mouse
  - Barcode reader
  - Scanner
  - Microphone
  - Touch screen
  - Digital camera
- (Any 2 × 1) (2)


- 6.3
- Chain printers
  - Drum printers
- (2)

6.4

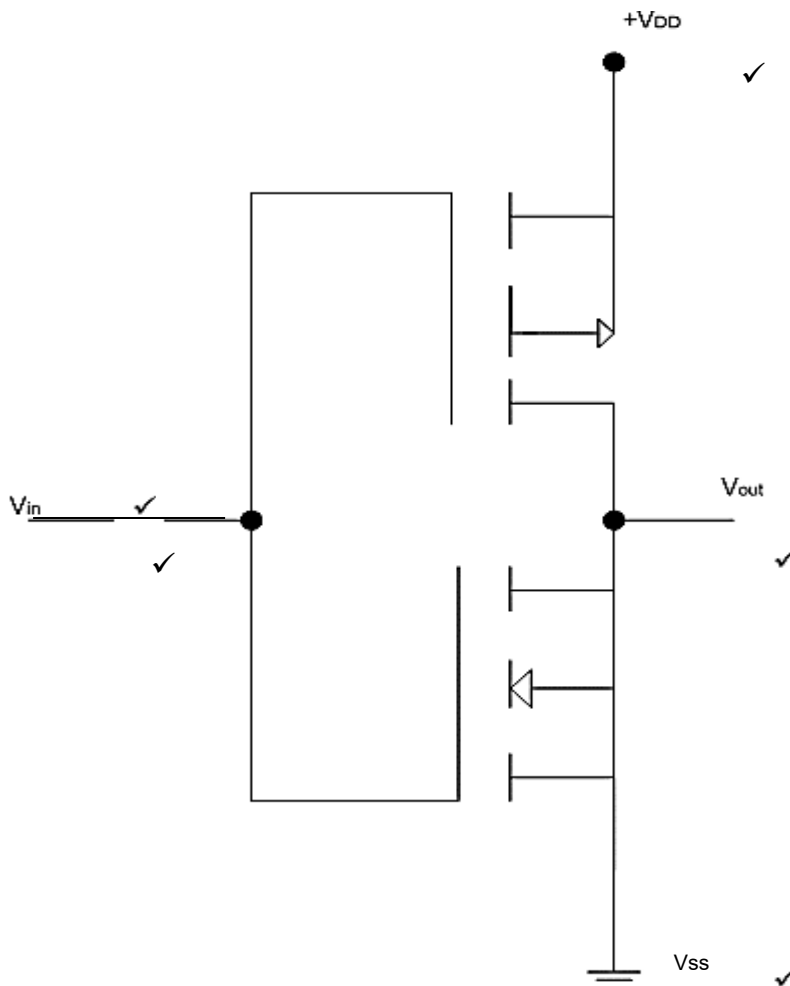

(NOTE: 1 × 3 for the correctness of the circuit.)  
 (1 × 2 for any TWO correct labels.) (5)  
**[11]**

QUESTION 7

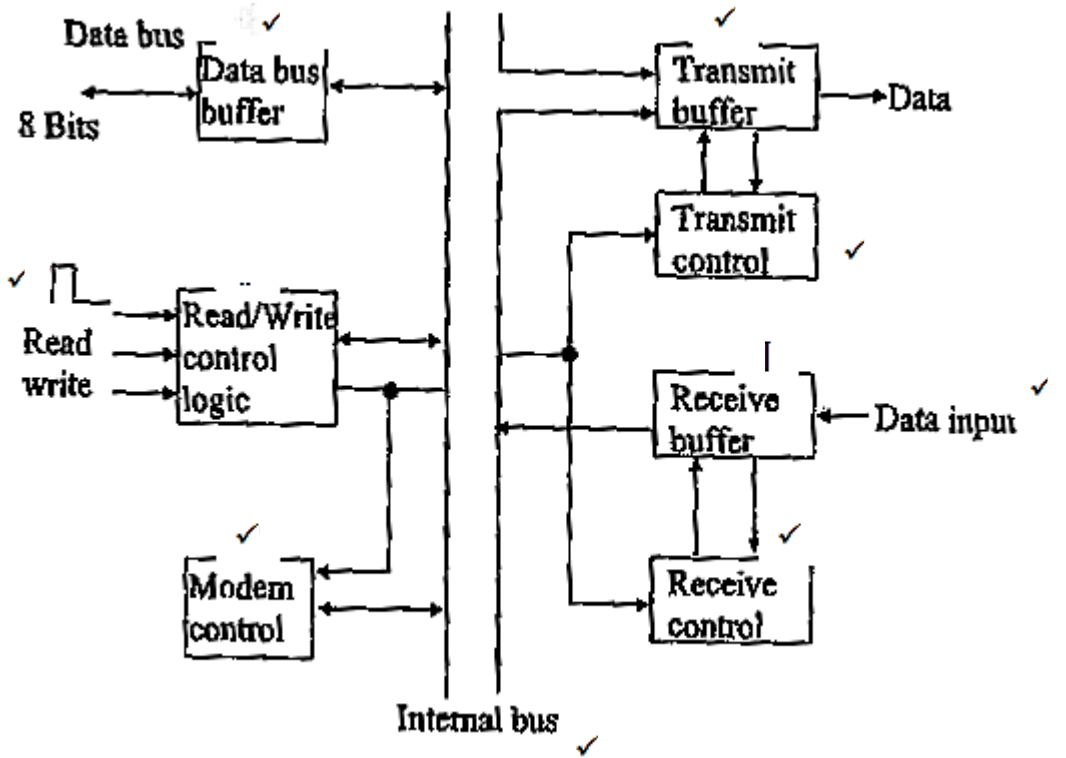

[8]

TOTAL: 100