



**higher education
& training**

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE

**NATIONAL CERTIFICATE
DIGITAL ELECTRONICS N5**

6 AUGUST 2019

This marking guideline consists of 9 pages.

QUESTION 1

1.1 $237,7_8 \div A,7_{16}$

$237,7_8 = 10011111,111_2 \checkmark$ {Each octal decimal is represented by 3 binary bits}

$A,7_{16} = 1010,0111_2$

$$\begin{array}{r}
 \sqrt{1001111111110,000} \\
 \underline{-10100111} \\
 100110001 \checkmark \\
 \underline{-10100111} \\
 100010101 \\
 \underline{-10100111} \checkmark \\
 011011100 \\
 \underline{-10100111} \\
 0011010100 \\
 \underline{-10100111} \\
 001011,010 \checkmark
 \end{array}$$

$\therefore 10011111,111_2 \div 1010,0111_2 = 1111,010_2 = 17,2_8 \checkmark$

1.2 $37,6_8 \times 10,01_2$

$37,6_8 = 011111,110_2 = 11111,11_2 \checkmark$ {Each octal decimal is represented by 3 binary bits}

$$\begin{array}{r}
 1111111 \\
 \times \quad \underline{1001} \\
 1111111 \checkmark \\
 +1111111000 \checkmark \\
 \hline
 \end{array}$$

Shift back the comma into three places $1000111,0111 \checkmark \checkmark$

$\therefore 37,6_8 \times 10,01_2 = 10010,001_2 = 47,7_{16} \checkmark$

1.3 $29,5_{10} - 21,7_8$

$29,5_{10}$

2^4	2^3	2^2	2^1	2^0	2^{-1}
1	1	1	0	1	1

$29,5_{10} = 11101,1_2 \checkmark$

$21,7_8 = 010\ 001,111 = 10001,111_2 \checkmark$ {each octal is represented by 3 binary bits}

11101,100		1 1 1 0 1, 1 0 0
-10001,111		+ 0 1 1 1 0, 0 0 1 \checkmark
There is carry		1 0 1 0 1 1, 1 0 0 \checkmark
Answer will be positive		0 1 0 1 1, 1 0 0
Add carry to the L.S.B		+1
		1 0 1 1, 1 0 1 \checkmark

Therefore $11101,1_2 - 10001,111_2 = 1011,101_2 = 11,625_2 \checkmark$

(3 × 6) [18]

QUESTION 2

2.1

A	B	C	D	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D	
0	0	0	0	0	X	0	X	0	X	1	1	✓
0	0	0	1	0	X	0	X	1	X	X	X	✓
0	0	1	0	0	X	0	X	X	0	1	1	✓
0	0	1	1	0	X	1	X	X	1	X	X	✓
0	1	0	0	0	X	X	0	0	X	1	1	✓
0	1	0	1	0	X	X	0	1	X	X	X	✓
0	1	1	0	0	X	X	0	X	0	1	1	✓
0	1	1	1	1	X	X	1	X	1	X	X	✓
0	0	0	0	X	0	0	X	0	X	1	1	✓
1	0	0	1	X	1	0	X	0	X	X	X	✓

1010	}	Don't cares (X's) ✓
1011		
1100		
1101		
1110		
1111		
1111		

(11)

2.2

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	0	0	X	X
$\bar{C}D$	0	0	X	X
CD	0	1	X	X
$C\bar{D}$	0	0	X	X

$J_A = BCD$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	X	X	X	0
$\bar{C}D$	X	X	X	1
CD	X	X	X	X
$C\bar{D}$	X	X	X	X

$K_A = D$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	0	X	X	0
$\bar{C}D$	0	X	X	0
CD	1	X	X	X
$C\bar{D}$	0	X	X	X

$J_B = CD$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	X	0	X	X
$\bar{C}D$	X	0	X	X
CD	X	1	X	X
$C\bar{D}$	X	0	X	X

$K_B = CD$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	0	0	X	0
$\bar{C}D$	1	1	X	0
CD	X	X	X	X
$C\bar{D}$	X	X	X	X

$J_C = \bar{A}D$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	X	X	X	X
$\bar{C}D$	X	X	X	X
CD	1	1	X	X
$C\bar{D}$	0	0	X	X

$K_C = D$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	1	1	X	1
$\bar{C}D$	X	X	X	X
CD	X	X	X	X
$C\bar{D}$	1	1	X	X


$J_D = 1$ ✓

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}\bar{D}$	X	X	X	X
$\bar{C}D$	1	1	X	1
CD	1	1	X	X
$C\bar{D}$	X	X	X	X

$K_D = 1$

(8)

2.3

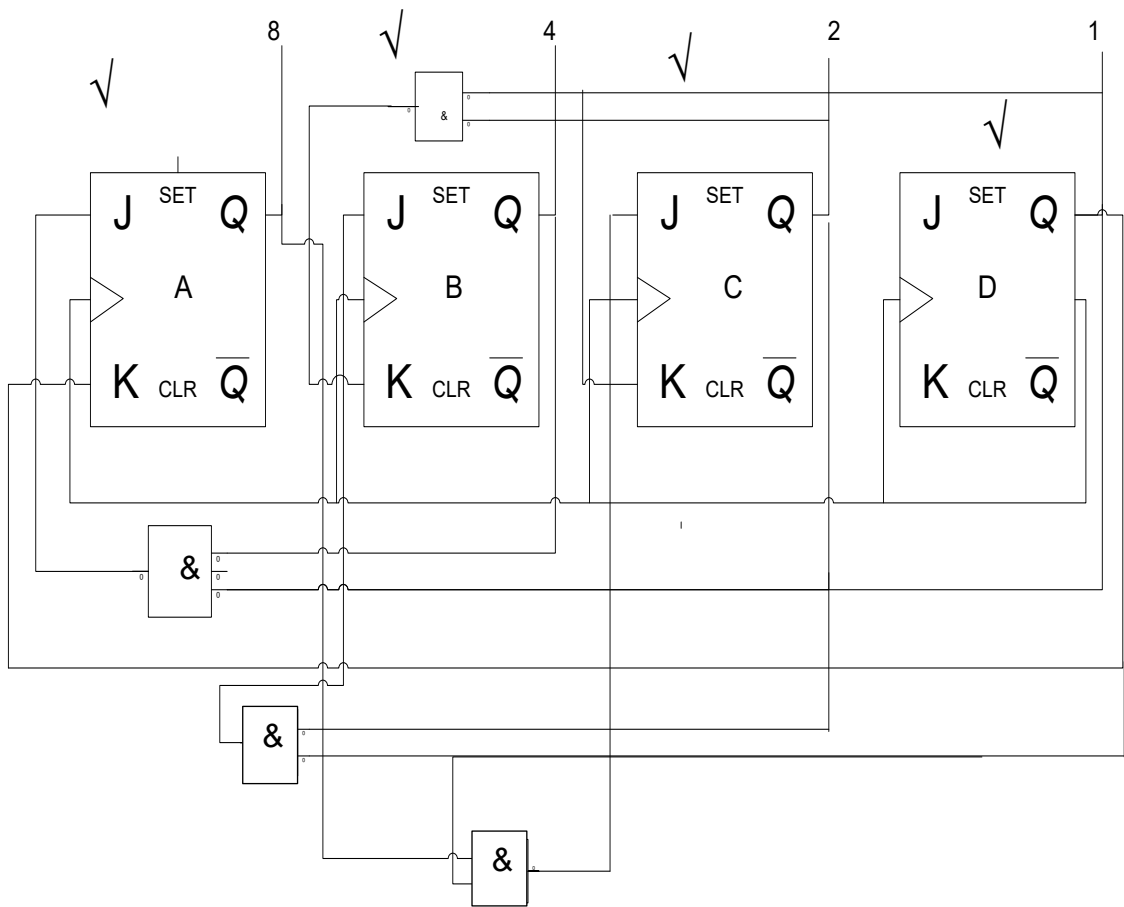


OR

(6)
 [25]

QUESTION 3

3.1

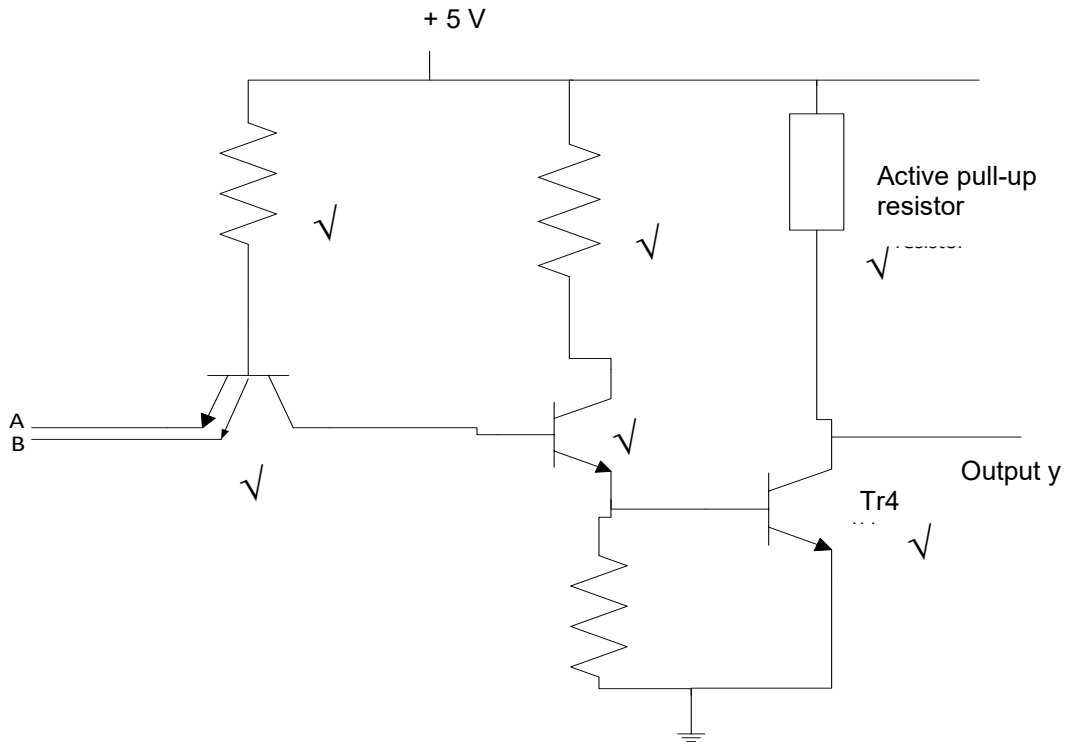

(6)


- 3.2
- Unused inputs should be connected to V_{CC} or ground. If left open, they will float to different levels.
 - Always use conductive foam when storing MOS devices.
 - Always place MOS devices with pins down on a ground surface.
 - Ensure that tools, benches are earth-grounded.
 - Never connect MOS devices with the power ON.

(5)

[11]

QUESTION 4

4.1

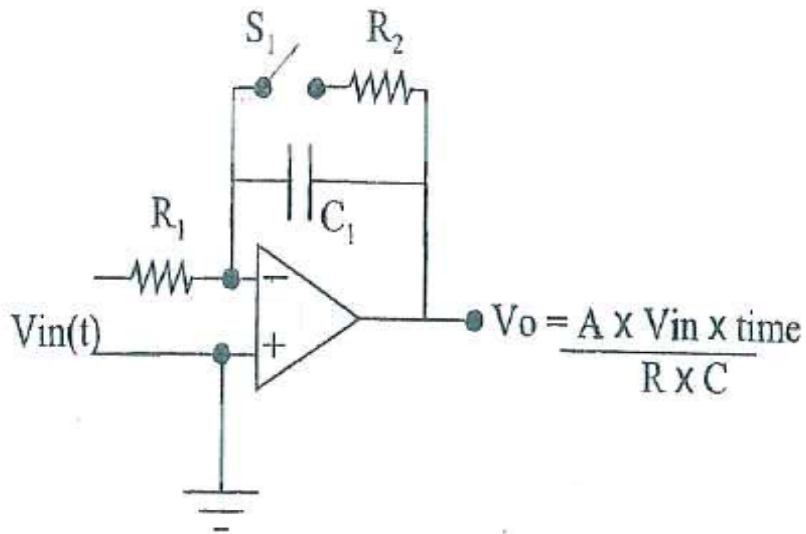

$$V_o = \frac{A \times V_{in} \times \text{time}}{RC} = \frac{1\,024 \times 2,8 \times 1,2 \times 10^{-3}}{200 \times 10^3 \times 250 \times 10^{-6}} = 0,069\text{ V}$$

(8)


4.2

- The process starts when the counter is RESET by circuitry.
- Counts will proceed from 0 in step-size format until $V_A = V_R$.
- The conversion time will vary, depending on the analogue input (V_A).
- As long as the reference voltage is less than the analogue input voltage, the output of the comparator will stay high. Put the counter in the UP-count mode, which causes the counter to produce an UP-sequence of binary counts.

(5)
[13]

QUESTION 5

5.1

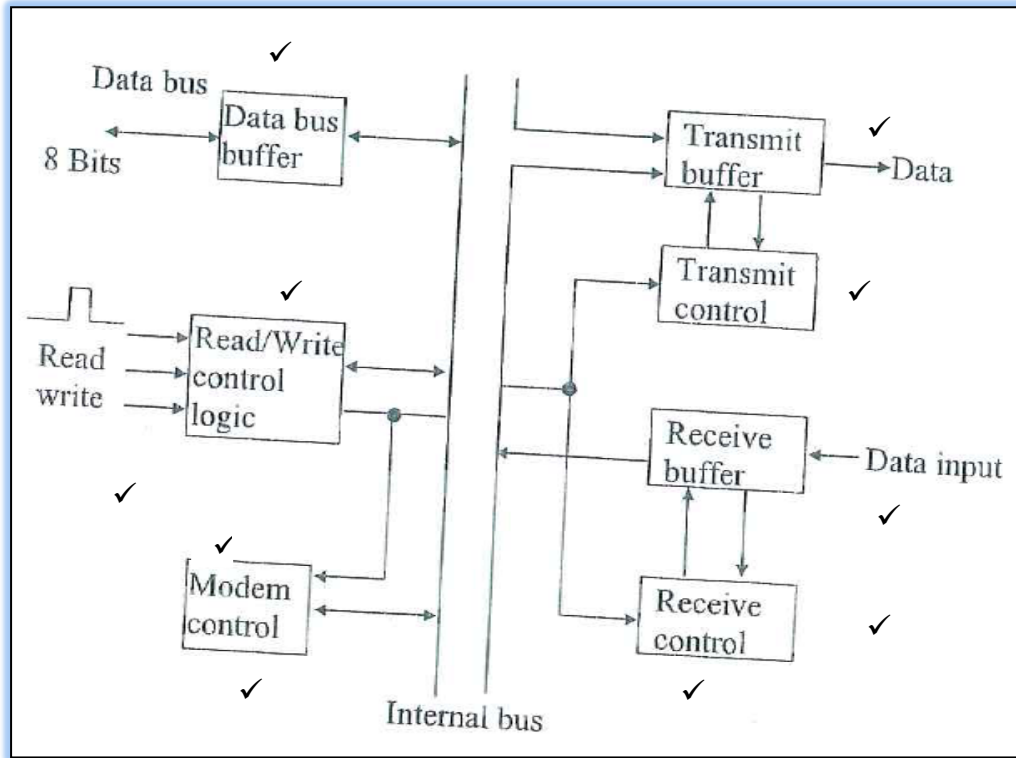

(10)

- 5.2
- 5.2.1 False
 - 5.2.2 False
 - 5.2.3 False
 - 5.2.4 True
 - 5.2.5 True

(5 × 1) (5)
[15]

QUESTION 6


- 6.1
- Keyboard
 - Mouse
 - Joystick
 - Image scanner
 - Light pen
 - Touch screen
 - Digital camera
 - Webcam
 - Graphic tablet
 - Microphone
 - Printer
 - Projector
 - Barcode reader
 - Game controller

(Any 3 × 1) (3)

6.2	6.2.1	A
	6.2.2	A
	6.2.3	D
	6.2.4	A
	6.2.5	C

(5 × 1) (5)
[8]

QUESTION 7

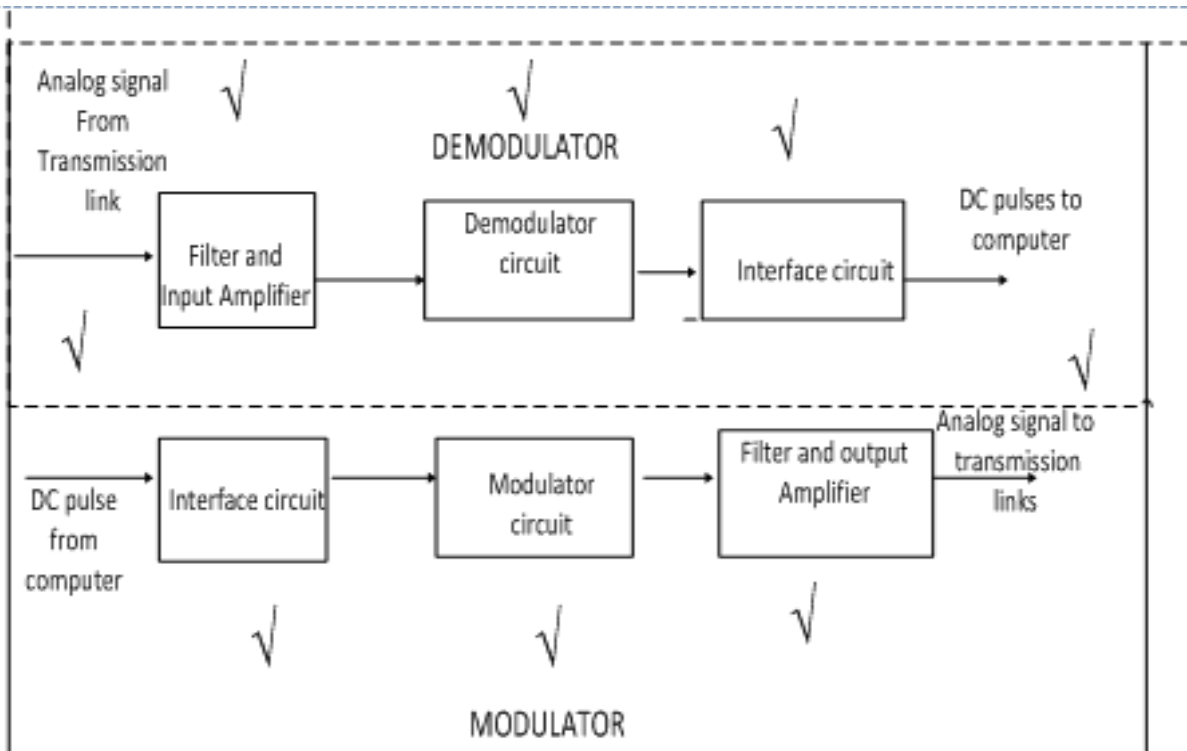

[10]

TOTAL: 100