



**higher education
& training**

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE

NATIONAL CERTIFICATE INDUSTRIAL ELECTRONICS N4

22 November 2022

This marking guideline consists of 7 pages.

QUESTION 1


1.1

$$V_{AB} = \frac{R_2}{R_1 + R_2} \times V_1 = \frac{1.1}{2 + 1.1} \times 6 = 2,129 \text{ V} \checkmark$$

$$V_{BA} = \frac{R_1}{R_1 + R_2} \times V_2 = \frac{2}{2 + 1.1} \times 9 = 5,806 \text{ V} \checkmark$$

$$V_{TH} = V_{AB} + V_{BA} = 2,129 + 5,806 = 7,935 \text{ V} \checkmark \checkmark$$
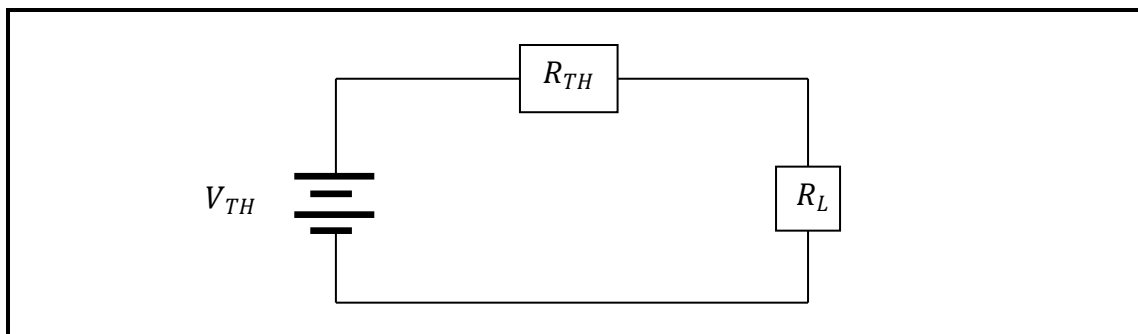
$$R_{TH} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{2 \times 1.1}{2 + 1.1} = 0,710 \Omega \checkmark \checkmark$$



$$I_{R_L} = \frac{V_{TH}}{R_{TH} + R_L} = \frac{7,935}{0,71 + 16} = 0,475 \text{ A} \checkmark \checkmark$$

(8)

1.2


- Remove the load resistor and label terminals A and B where the load is removed.
- Calculate V_{TH} that appears across these terminals.
- Short-circuit all voltage sources and open-circuit all current sources.
- Calculate R_{TH} between both terminals A and B.
- Draw the Thevenin equivalent circuit with V_{TH} and R_{TH} .
- Insert the load resistor between terminals A and B.
- Calculate the required current/voltage.

(Any 2 × 1)

(2)
[10]

QUESTION 2

2.1

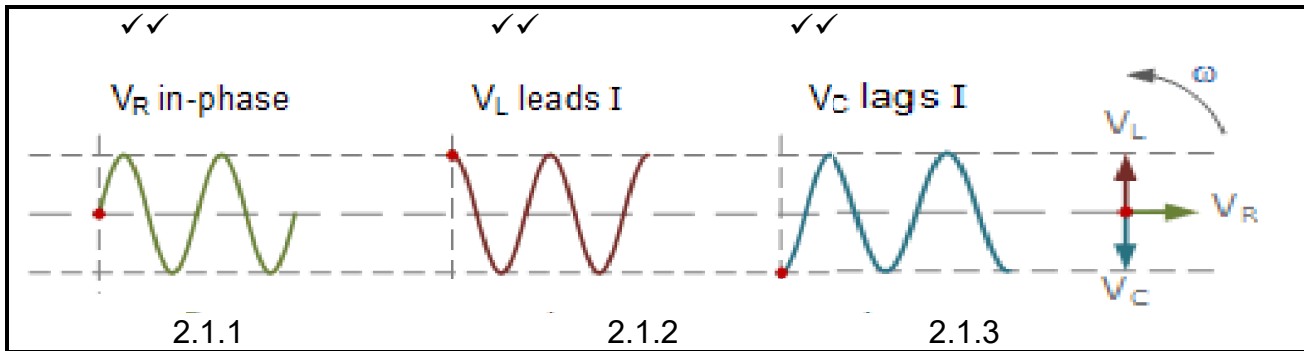

(3 × 2)

(6)

2.2

$$BW = f_H - f_L = \Delta f = \frac{f_r}{Q} = \frac{5 \times 10^6}{250} = 20 \text{ kHz}$$

$$f_L = f_r - \frac{\Delta f}{2} = 5 \times 10^6 - \frac{20 \times 10^3}{2} = 4,990 \text{ MHz}$$

$$f_H = f_r + \frac{\Delta f}{2} = 5 \times 10^6 + \frac{20 \times 10^3}{2} = 5,010 \text{ MHz}$$

(3)

2.3

$$2.3.1 \quad Z_A = \frac{V_S}{I_A} = \frac{100 \angle 0^\circ}{10 \angle 0^\circ} = 10 \angle 0^\circ$$

$$2.3.2 \quad Z_B = \frac{V_S}{I_B} = \frac{100 \angle 0^\circ}{13,426 \angle -147,5^\circ} = 7,448 \angle 147,5^\circ$$

$$2.3.3 \quad Z_C = \frac{V_S}{I_C} = \frac{100 \angle 0^\circ}{5,614 \angle 63,3^\circ} = 17,813 \angle -63,3^\circ$$

(3 × 2)


(6)

[15]

QUESTION 3

3.1

3.1.1

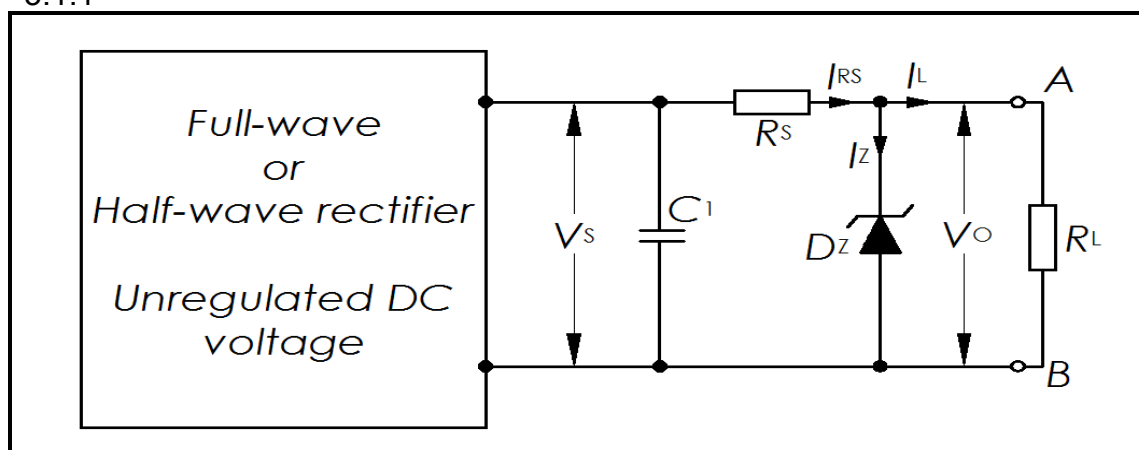

(3)

- 3.1.2
- If the current through RL increases, the Zener current will fall with the corresponding amount.
 - If the load current through RL decreases, the Zener current will increase with the corresponding amount.
- (2)

3.2

$$V = \frac{kT}{q} \ln \left(\frac{i}{I_s} + 1 \right) = \frac{1,38 \times 10^{-23} \times (273 + 17)}{1,6 \times 10^{-19}} \ln \left(\frac{1,5 \times 10^{-3}}{12 \times 10^{-6}} + 1 \right) = 0,121 \text{ V}$$


(3)

- 3.3
- Varactor diodes make less noise compared to other conventional diodes.
 - They are available at low cost.
 - The varactor diodes are small in size and therefore very lightweight.
 - Varactor diodes are more reliable.
 - Varactor diodes have no purpose when operated in forward bias.
 - An increase in the reverse bias of varactor diodes causes an increase in the capacitance.
- (Any 2 × 1)
- (2)

[10]**QUESTION 4**

- 4.1 4.1.1 Full (1)

4.1.2

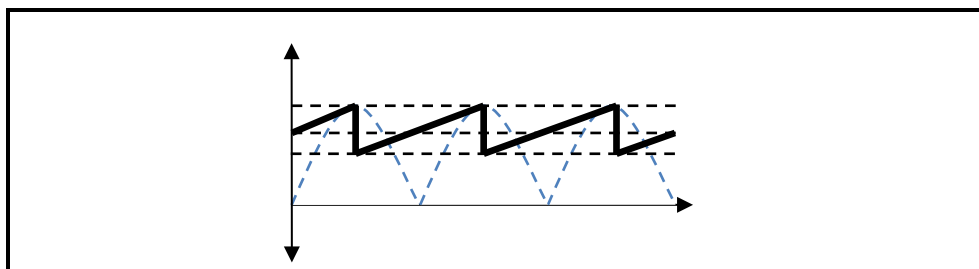

(2)

4.1.3

$$V_{dc} = V_p - \frac{I_{dc}}{4fC} = 15 - \frac{10 \times 10^{-3}}{4 \times 50 \times 30 \times 10^{-6}} = 10 \text{ V}$$

(3)

4.1.4

$$V_{r(rms)} = \frac{I_{dc}}{4\sqrt{3}fC} = \frac{10 \times 10^{-3}}{4 \times \sqrt{3} \times 50 \times 10 \times 10^{-6}} = 2,887 \text{ V}$$

(3)

4.1.5

$$R_L = \frac{V_{dc}}{I_{dc}} = \frac{10}{10 \times 10^{-3}} = 1 \text{ k}\Omega$$

(2)

- 4.2
- Step-up transformer
 - Autotransformer
 - Step-down transformer
 - Isolation transformer
- (Any 2 × 1)
- (2)

- 4.3 Is the process of converting an alternating voltage to a unidirectional voltage. (2)

[15]

QUESTION 5


5.1 It is a semiconductor device consisting of two PN junctions. (1)

5.2 5.2.1 Static values are calculated when a transistor has no AC signal, i.e. the values are calculated at the Q-point in the steady-state.

5.2.2 Dynamic values are calculated when there is an AC input signal applied to the amplifier, i.e. the values are calculated as the parameters change for a corresponding changing AC input signal.

(2 × 2) (4)

5.3

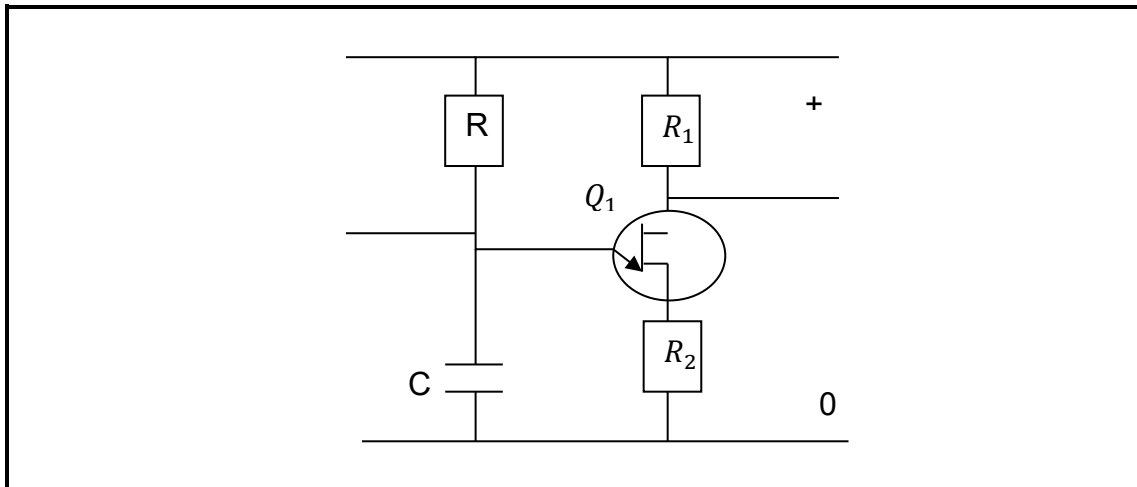

(4)

5.4 5.4.1 False
5.4.2 True
5.4.3 True
5.4.4 True
5.4.5 False

(5 × 1) (5)
[14]


QUESTION 6

6.1 F
6.2 A
6.3 E
6.4 B
6.5 C

(5 × 2) **[10]**

QUESTION 7

7.1

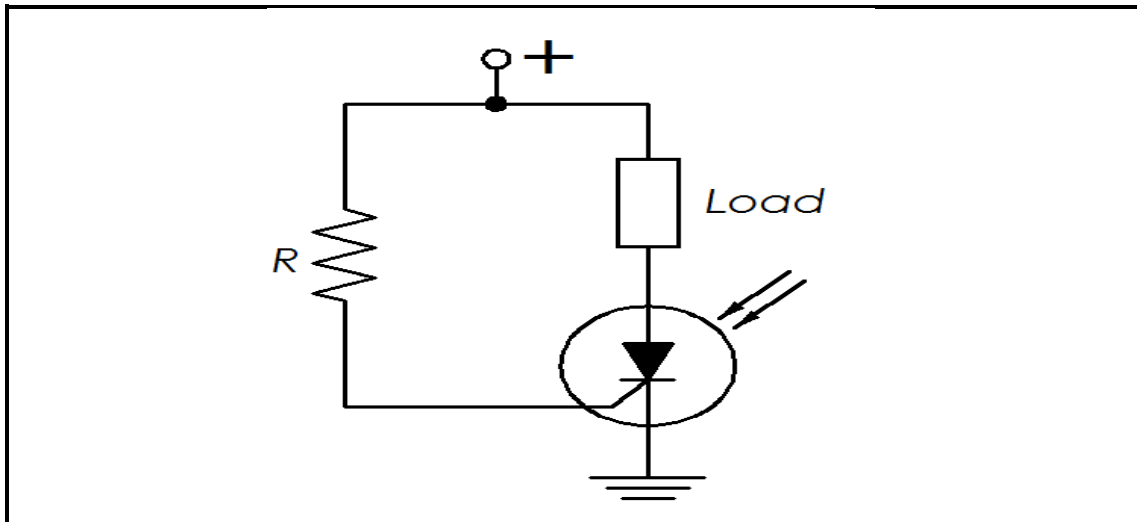


(3)

- When no light is present, the LASCR is off, no current flows through the load.
- When the light activates the LASCR, it turns on, allowing current to flow through load.
- The resistor is used to set the triggering level of the LASCR.


(3)

7.2

7.2.1

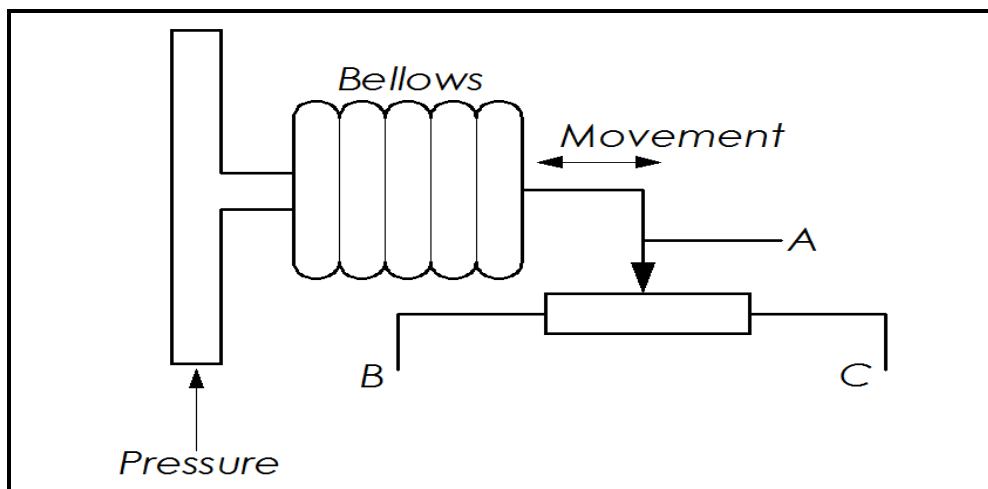

7.2.2

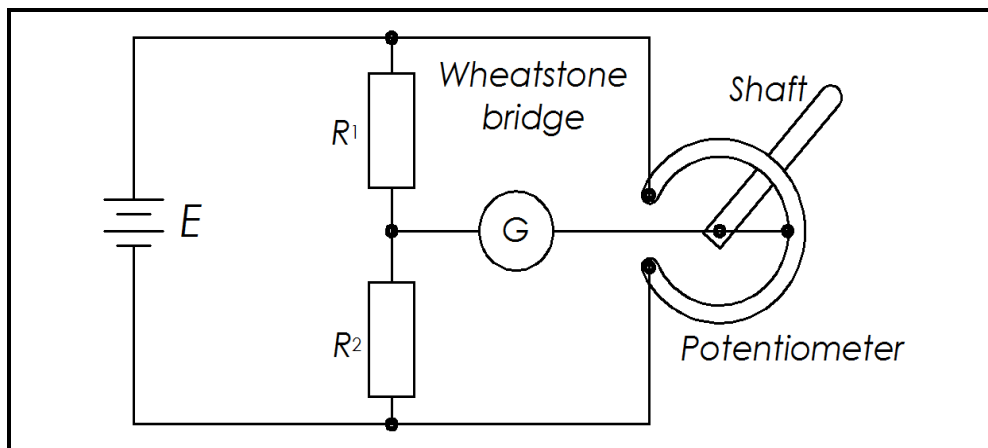

(2 × 4)

(8)

- 7.3
- Resistive
 - Capacitive
 - Inductive
 - Photo-sensitive
- (Any 2 × 1) (2)
- [16]**

QUESTION 8

- 8.1 8.1.1 $V_{in} = \text{no. of divs} \times \frac{\text{volts}}{\text{div}} = 3 \times 4 = 12 \text{ V}$ (2)
- 8.1.2 $t = \text{no. of divs} \times \frac{\text{time}}{\text{div}} = 8 \times 2 \times 10^{-6} = 12 \mu\text{sec}$
- $f = \frac{1}{t} = \frac{1}{12 \times 10^{-6}} = 83,333 \text{ kHz}$ (4)
- 8.2
- Sine wave
 - Square wave
 - Triangular (sawtooth) wave
- (Any 2 × 1) (2)
- 8.3
- Gas focusing
 - Electrostatic focusing
 - Electromagnetic focusing
- (Any 2 × 1) (2)
- [10]**

TOTAL: 100