

MOTOR CONTROL
AUTOMATIC SEQUENCE STARTER

RELAY LOGIC

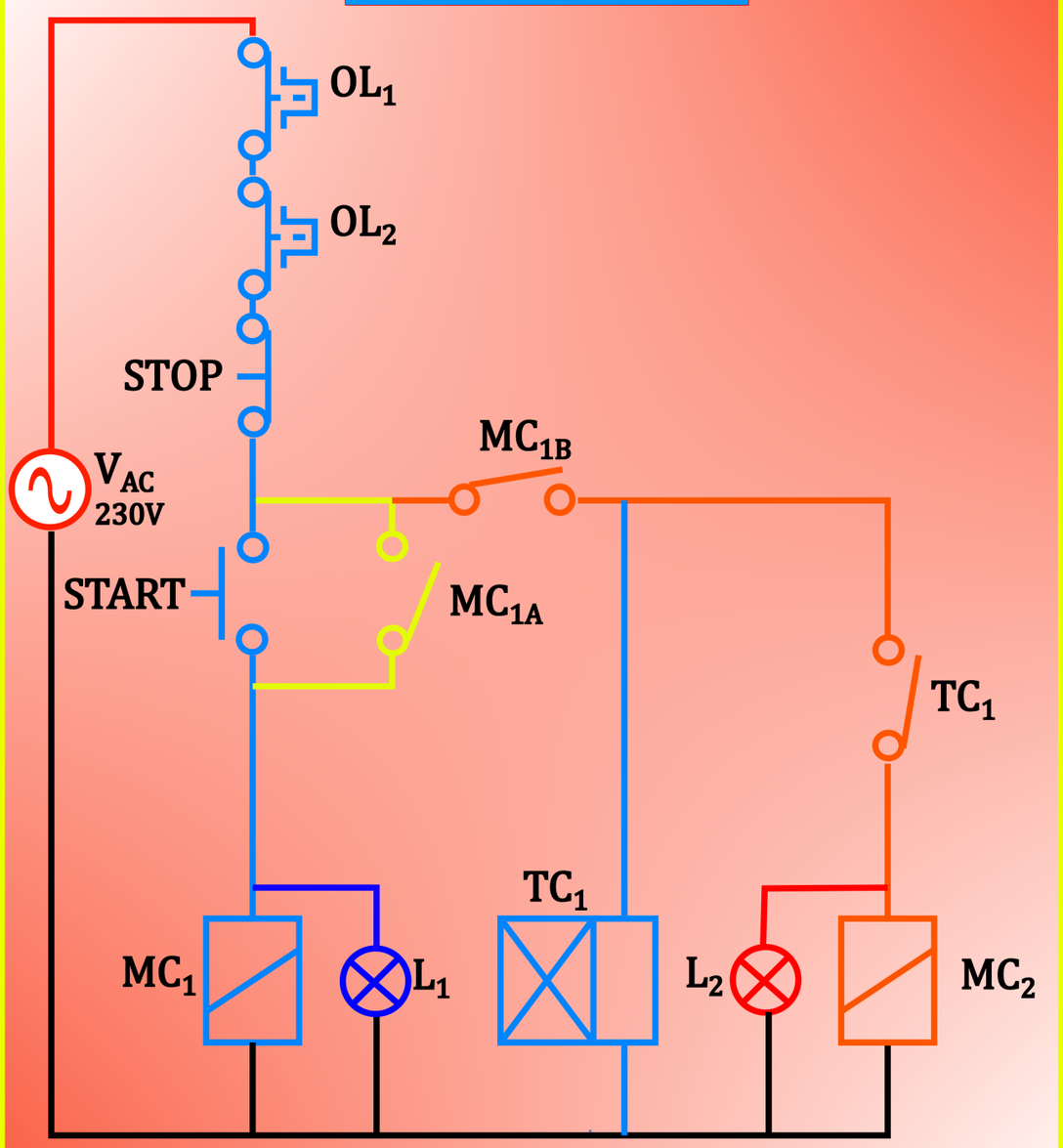


CONTROL

RELAY LOGIC

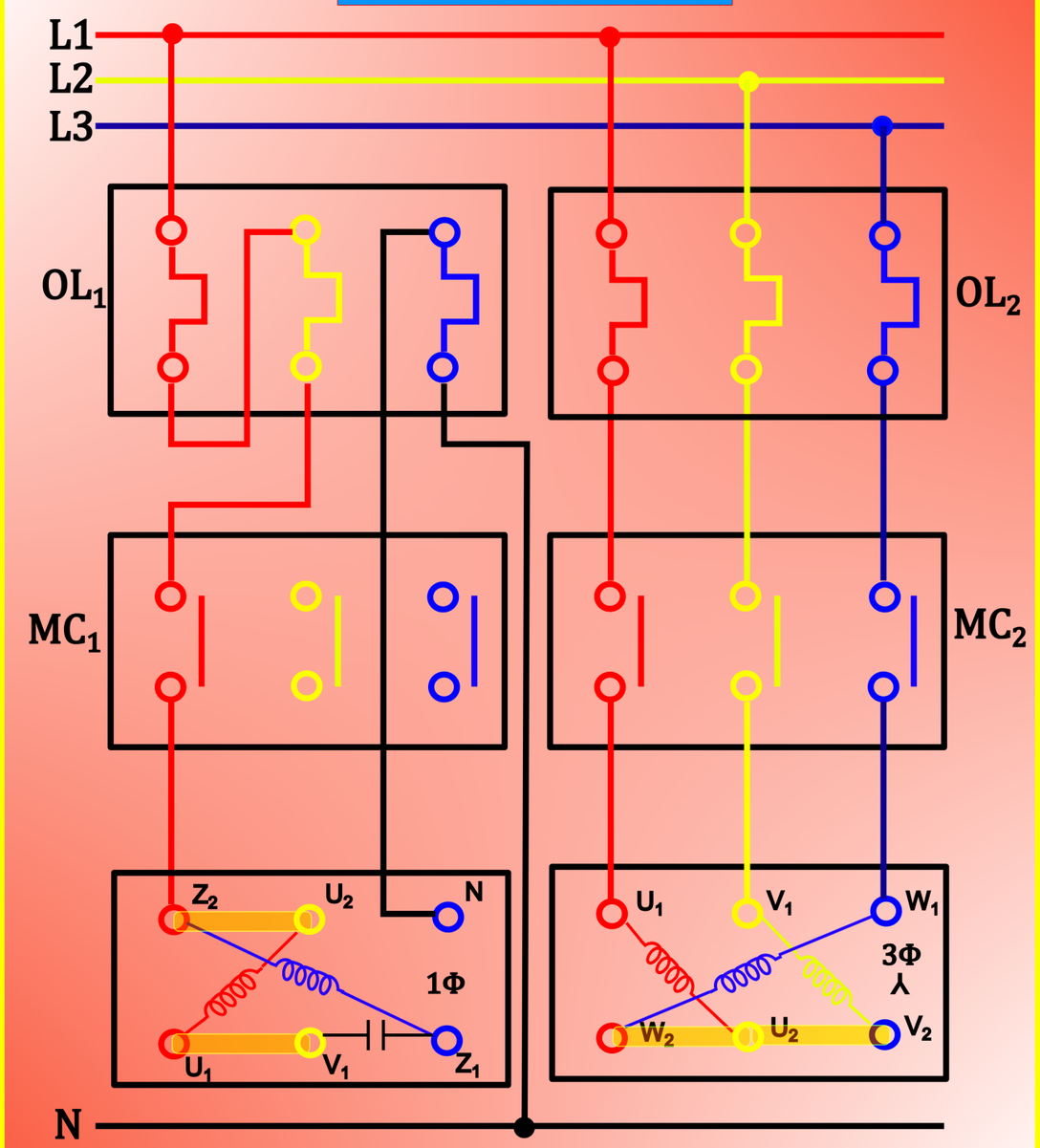


POWER

LADDER LOGIC

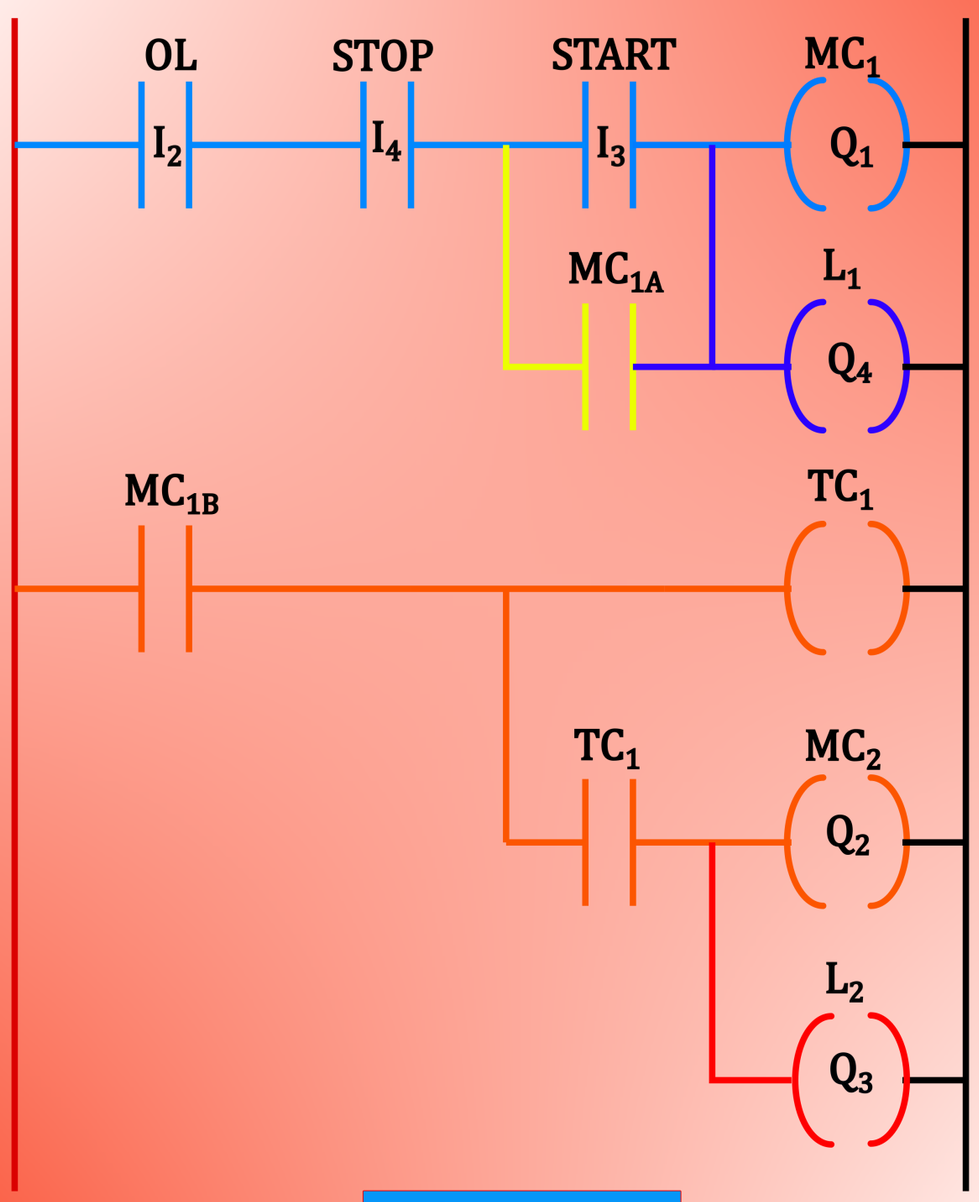

CONTROL

PROGRAMMABLE LOGIC CONTROLLER (PLC)

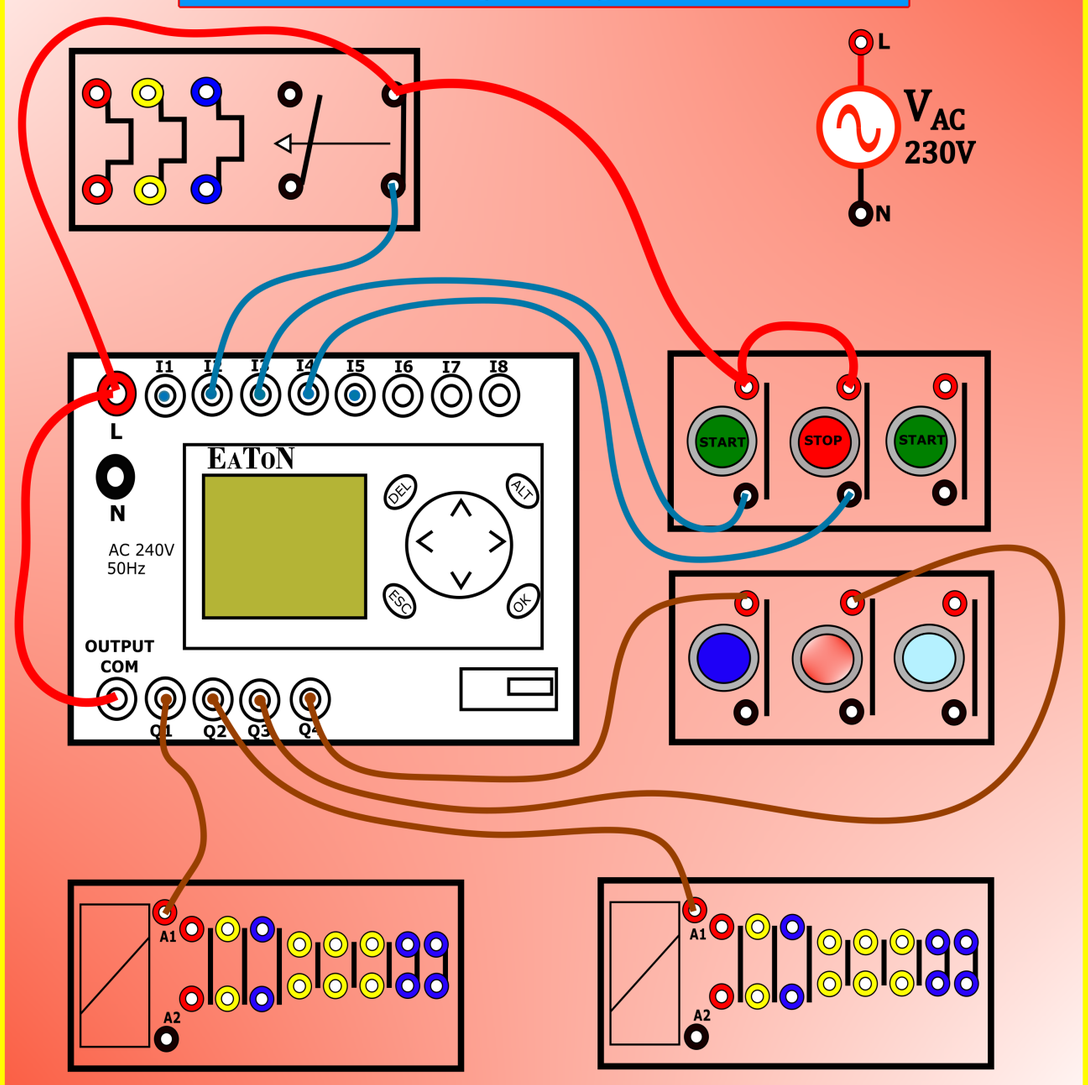

Scan the QR for a description of the circuit.

Western Cape Government
Education